



COMSATS University Islamabad, Vehari Campus
Department of Computer Science
Final Paper Spring-19

Class: BSCS/BSSE
Subject: Digital Logic Design
Total Time Allowed: 3 Hours.
Name: AHMER IQBAL


Date: 17-06-2019
Instructor: M Rehan Ashraf
Max Marks: 50
Registration# SP18-BSE-002

Note: Attempt all questions, be specific and to the point. Clearly show the detail of your work.

Q#01: Short Questions

 - a) Design a combinational logic circuit that has four inputs and one output. The output is equal to 1, when input is greater than 1000. (2)
- b) Implement $Y=AB+CD$ using NAND gates only. (2)
- c) Differentiate the following (2)
 - 1) Latch Vs Flip Flop, 2) Sequential Circuits Vs Combinational Circuits
 - 3) Analog Devices Vs Digital Devices, 4) Volatile Vs Nonvolatile memory
- d) Why the gates are called decision making elements? How many input signals can a gate have? How many output signals? (2)
- e) What is the main difference between inverter and controlled inverter? Show the circuit diagram of a controlled inverter. (2)
- f) Define the following (2)
 - Chunking, Propagation Delay Time, Setup Time, Hold Time

- Q#02: a) Draw the circuit diagram of a negative edge triggered JK flip flop. (2)
- b) Draw the output of the positive edge triggered flip flop for the inputs given below. Clearly show the timing diagram of output for all the possible states. (6)



- Q#03: a) Design a synchronous/asynchronous down counter which counts from 15 to 0. (7)
Clearly show the timing diagram of all the states.


(Handwritten signature)

- b) Modify the designed counter in part a so that it starts from 7 and down counts up to 0. (5)
- Q#04: Use the Karnaugh Map method to implement the minimum SOP expression for the logic function specified in the truth table given below. (8)

$$Y = \bar{A}C + \bar{A}D + BD + A\bar{B}\bar{D}$$

	A	B	C	D	F
0	0	0	0	0	0
1	0	0	0	1	1
2	0	0	1	0	1
3	0	0	1	1	1
4	0	1	0	0	0
5	0	1	0	1	1
6	0	1	1	0	1
7	0	1	1	1	1
8	1	0	0	0	1
9	1	0	0	1	0
10	1	0	1	0	1
11	1	0	1	1	0
12	1	1	0	0	0
13	1	1	0	1	1
14	1	1	1	0	0
15	1	1	1	1	1

 - Q#05: a) Draw the circuit diagram of a hexadecimal encoder. (5)
- b) Calculate the output of the circuit given below for all input combinations. (5)



GOOD LUCK

Handwritten signature