



COMSATS Institute of Information Technology Vehari

Department of Computer Science

First Sessional EXAMINATION – Spring 2018

Class: BSSE-B10

Subject: Electric Circuit Analysis

Time Allowed: 90 min.

Name: AHMED TORAL


Date: 20-03-2018

Instructor: M. Rehan Ashraf


Max Marks: 10

Registration # SP18-BSE-002

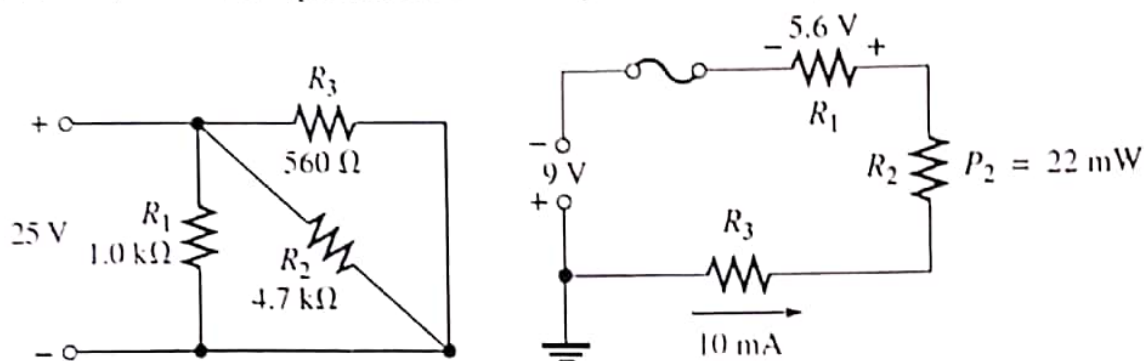Q#01: Find the unknown quantities in the circuit given below? (2+3)



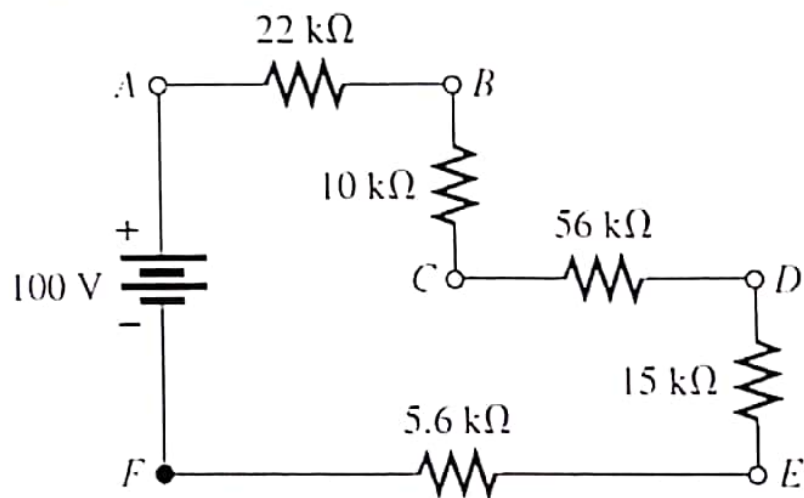Q#02: Find the voltage at the indicated points in the figure given below. Assume the ground is connected at point C. (5)



Good Luck

Rehan Ashraf