



COMSATS Institute of Information Technology Vehari

Department of Computer Science

2nd Sessional EXAMINATION – Spring 2018

Class: BSSE-B10

Subject: Electric Circuit Analysis

Time Allowed: 90 min.

Name: Ahmer Iqbal

Date: 03-05-2018



Instructor: M. Rehan Ashraf

Max Marks: 15

Registration # SP18-BSE-002



Q#01: Determine the Thevenin equivalent as seen from the terminals A and B. (5)

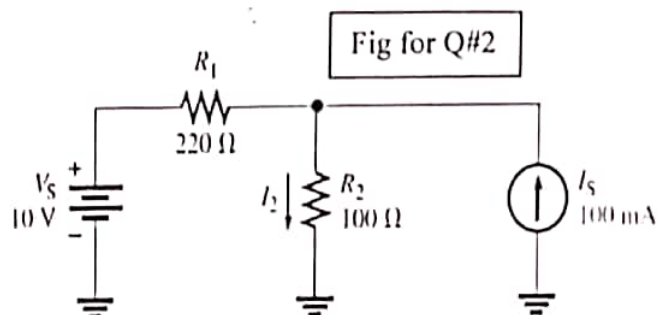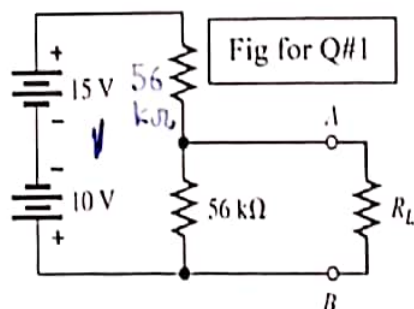Q#02: Find the current through R_2 in the circuit given below. (4)



Q#03: Find the voltage drop and current through each resistor in the figure given below, also find the total applied voltage. (4)

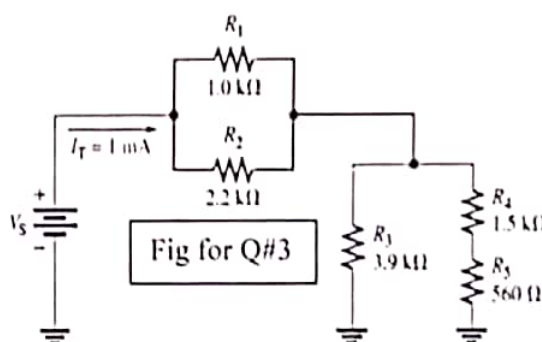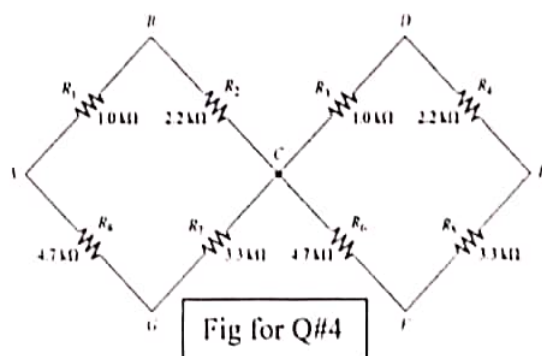Q#04: Find R_{AB} , R_{BC} , R_{CD} and R_{AE} . Only expressions are required, no need of exact values. (2)



Good Luck

Raymond